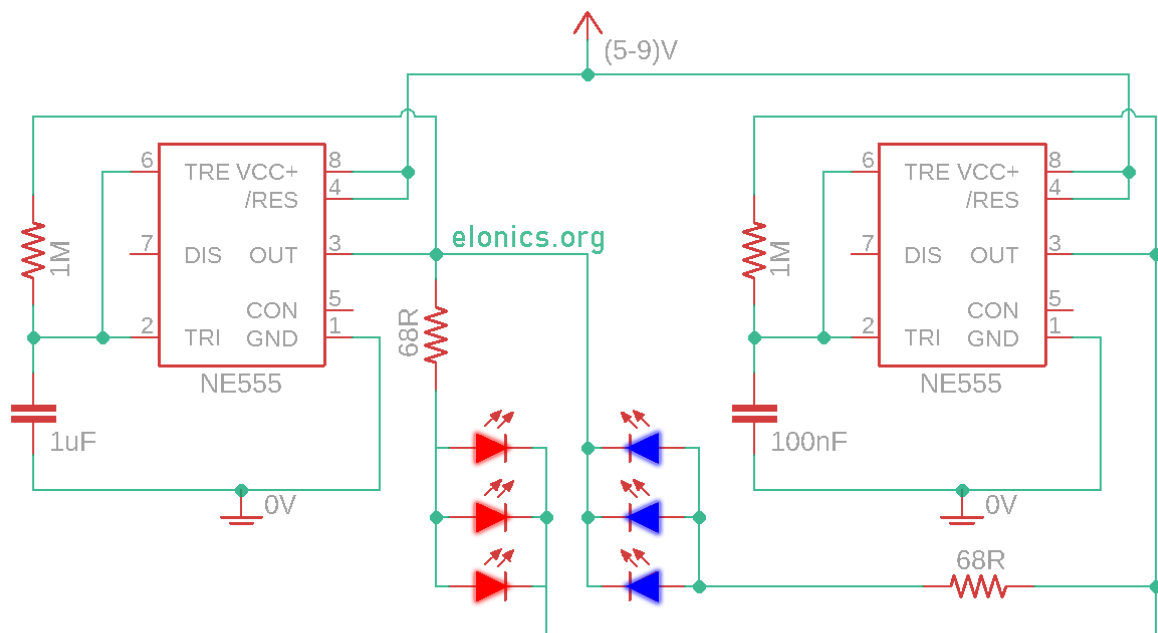


## Flashing Police Light LED Effect using 555 Timer IC

### COMPONENT :

- 2 x 555 Timer ICs
- LED's: 3 x Red, 3 x Blue
- Resistors: 2 x 1M, 2 x 68R (Resistors for LED's)
- Capacitors: 1uF, 100nF
- Breadboard
- Few Breadboard Connectors
- (5-12)V Power Supply

### BLOCK / CIRCUIT DIAGRAM :



## POLICE LIGHTS LED FLASHER CIRCUIT

